

PH 222-2A

02/26/2022

RECITATION #7

NAME :- SHREYAS SRINIVASA

BLAZER ID :- SSRINI VA

Ans. The ~~equivalent~~ equivalent capacitance of the capacitors when they are connected in parallel combination is as follows:- $C_{eqn} = C_1 + C_2$, where

C_1 & C_2 are the capacitances of the capacitors 1 & 2.

The equivalent capacitance of the capacitors when they are connected in series combination is as follows:

$$\frac{1}{C_{eqn}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eqn} = \frac{C_1 C_2}{C_1 + C_2}$$

The capacitance of the capacitor is:-

$$C = \frac{Q}{V}$$

(2)

where Q is the charge on the capacitor and V is the voltage across the capacitor.

The sum of voltage around a closed conducting loop in a circuit must be zero. [\therefore Kirchhoff's loop rule]

$$\sum V = 0$$

When two capacitors C_1 & C_2 are connected with voltage source V , then voltage across the capacitor C_1 is as follows:-

$$V_{C_1} = \frac{C_2 V}{C_1 + C_2}$$

The voltage across the capacitor C_2 is:- $V_{C_2} = \frac{C_1 V}{C_1 + C_2}$

(a) The capacitors $4 \mu F$ and $2 \mu F$ are

(3)

connected in series when the switch is open. The voltage across the capacitor $C_1 = 4 \mu F$ is

$$V_{C_1} = \frac{C_2 V}{C_1 + C_2}$$

substituting $4 \mu F$ for C_1 , $2 \mu F$ for C_2 and $300V$ for V , we get:-

$$V_{C_1} = \frac{2 \mu F}{2 \mu F + 4 \mu F} \times 300V$$

$$= 100V \quad \left[\because \frac{2}{6} \times 300 = 100 \right]$$

The voltage across the capacitor C_2 is:-

$$V_{C_2} = \frac{C_1 V}{C_1 + C_2}$$

(4)

substituting 4 μF for C_1 , 2 μF for C_2 ,
 & 300V for V , we get:-

$$V_{C_2} = \frac{4 \mu\text{F}}{2 \mu\text{F} + 4 \mu\text{F}} \times 300\text{V}$$

$$= \underline{\underline{200\text{V}}} \quad \left[\because \frac{4^2 \times 100}{6 \times 21} \right]$$

Using Kirchhoff's loop rule for the
 circuit across the junctions B & D in
 the figure in the question:-

$$-V_{C_1} - (V_E - V_D) + V_{C_2} = 0$$

$$V_E - V_D = V_{C_2} - V_{C_1}$$

Substituting 100V for V_{C_1} and
 200V for V_{C_2} , we get:-

$$\begin{aligned} V_E - V_D &= 200\text{V} - 100\text{V} \\ &= \underline{\underline{100\text{V}}} \end{aligned}$$

(5)

∴ the potential difference $V_E - V_0$
is 100 V

(2a) The capacitors $4 \mu F$ and $2 \mu F$ are connected in parallel on both sides when the switch is closed.

$$C_{24} = 4 \mu F + 2 \mu F$$

$$= 6 \mu F$$

As the voltage across the point E is

$$V_E = \left(\frac{C_{24}}{C_{24} + C_{24}} \right) V$$

Substituting $6 \mu F$ for C_{24} and $300 V$ for V , we get:-

$$V_E = \left(\frac{6 \mu F}{6 \mu F + 6 \mu F} \right) \times 300 V$$

$$= \underline{\underline{150 V}}$$

(6)

∴ The potential at point E after switch is closed is 150V.

(c) The capacitors $4\mu F$ and $2\mu F$ are connected in parallel on both sides, when the switch is closed.

$$C_{24} = 4\mu F + 2\mu F$$

$$= 6\mu F$$

Now, the two capacitors C_{24} are connected in series combination. Hence, their equivalent capacitance is as follows:-

$$C_{eq} = \frac{C_{24} \times C_{24}}{C_{24} + C_{24}}$$

$$= \frac{C_{24}}{2}$$

(7)

Substituting $6 \mu F$ for C_2 , we get

$$C_{eq} = \frac{3 \mu F}{2} = 1.5 \mu F$$

The charge passing through the switch is

$$Q = C_{eq} \cdot V$$

Substituting $1.5 \mu F$ for C_{eq} and $300V$

for V , we get

$$Q = 1.5 \mu F \left(\frac{1 \mu F}{10^6 \mu F} \right) \times 300V$$

$$= 9 \times 10^{-4} C$$

\therefore The charge passing through the switch is $9 \times 10^{-4} C$