

NAME :- SHREYAS SRINIVASA  
BLAZER ID :- SSRINIVA

03/29/2022

## EXAM #2

PH 222-2A

1. Ans answer is option C - Bulb A will be off and bulb B will be brighter.

When switch is open, current will pass through bulb A and then B, but when switch is closed, current will pass through the switch instead of bulb A, then through bulb B because greater current flows through region with low resistance, since the switch closed provides no resistance, all the current from the source passes through the switch and no current flows through bulb A so bulb A is off. The bulb B will become brighter as all the current passes through bulb B after passing through the closed switch.


2. Ans. Answer is option A - No resistors are connected in series.

All the three resistors are in parallel combination. If we apply Kirchhoff's Voltage law in any direction and in any loop, the current is not the same. In all three resistors, current is different.

(2)

3. Ans.

The given circuit is as follows:-

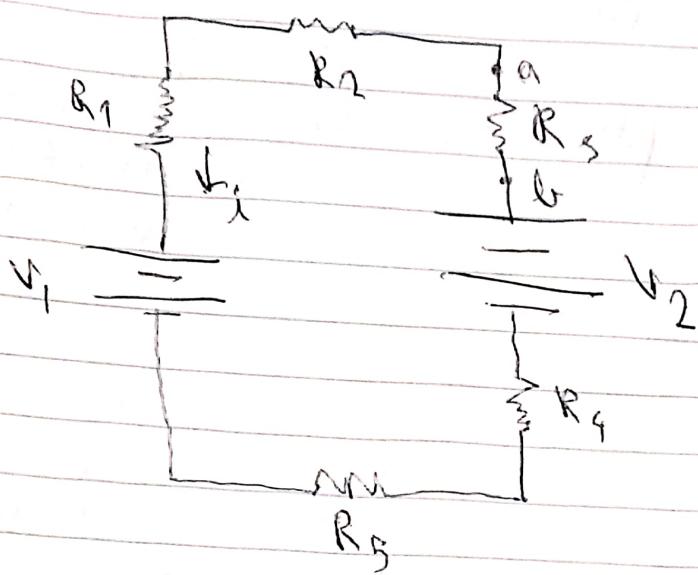

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 5 \text{ k}\Omega$$

$$R_3 = 15 \text{ k}\Omega$$

$$R_4 = 10 \text{ k}\Omega$$

$$R_5 = 5 \text{ k}\Omega$$

$$V_1 = 10 \text{ V}$$

$$V_2 = 20 \text{ V}$$

where  $i$  is the current flowing through the battery  $V_1$ .

Applying KVL in loop:-

$$V_1 = -iR_1 - iR_2 - iR_3 + V_2 + iR_4 - iR_5$$

$$10 = -i(10 + 5 + 15 + 10 + 5)$$

$$i = \frac{-10}{45} \text{ mA}$$

(3)

i.  $i_3 = -0.222 \text{ mA}$


Power on Resistor  $R_3 = I^2 R_3$

Here  $I =$  current through resistor  $R_3$ .



$$P = \left(\frac{10}{45}\right)^2 15 = 0.74 \text{ mWatt.}$$

$$P = 0.74 \text{ mW}$$

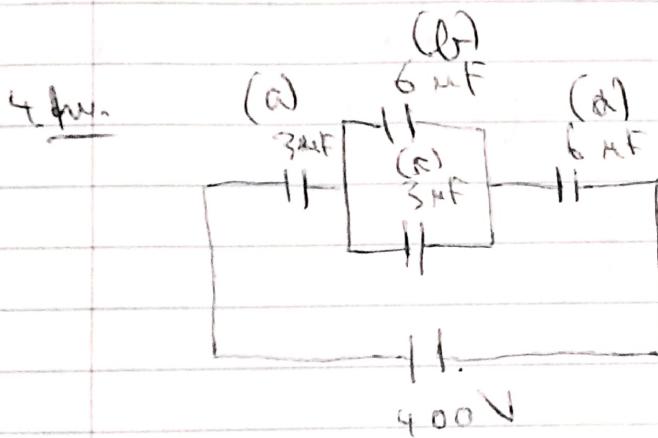

Let  $3 \mu\text{F}$  be (a),  $6 \mu\text{F}$  be (b),  $3 \mu\text{F}$  be (c) and  $6 \mu\text{F}$  be (d).

$$C_{eq} = 6 + 3 = 9 \mu\text{F} \text{ (for parallel)}$$

$$\frac{1}{C_{eq}} = \frac{1}{9} + \frac{1}{3} + \frac{1}{6} = \frac{2+6+3}{18}$$

3	4	3	6
3	5	1	2
2	1	1	2
1	1	1	1
1	8		

(4)

$$C_{\text{eq}} = \frac{18}{71} \mu F \text{ (for series)}$$

(A) Total energy =  $\frac{1}{2} C_{\text{eq}} V^2 = \frac{1}{2} \times \frac{18}{71} \times 400 \times 400 \times 10^{-6}$

$$= 1.3 \times 10^{-1}$$

Ans. The equivalent capacitance of the capacitor when they are in parallel combination is as follows:-

$$C_{\text{eq}} = C_1 + C_2$$

The equivalent capacitance of the capacitor when they are connected in series combination is as follows :-

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$

Capacitance of the capacitor is

$$C = \frac{Q}{V}$$

According to Kirchhoff's loop rule,

(4)

$$\sum V = 0$$

When two resistors  $C_1$  and  $C_2$  are connected with voltage source  $V$ , then voltage across the capacitor  $C_1$  is as follows:

$$V_{C_1} = \frac{C_2 V}{C_1 + C_2}$$

The voltage across the capacitor  $C_2$  is:

$$V_{C_2} = \frac{C_1 V}{C_1 + C_2}$$

(Q) The capacitors 4  $\mu F$  and 2  $\mu F$  are connected in series when switch is open. The voltage across the capacitor  $C_1 = 4 \mu F$  is 1,

$$V_{C_2} = \frac{C_2 V}{C_1 + C_2}$$

Substituting 4  $\mu F$  for  $C_1$ , 2  $\mu F$  for  $C_2$  and 300V for  $V$ , we get -

$$V_{C_1} = \left( \frac{2 \mu F}{2 \mu F + 4 \mu F} \right) \times 300V = 100V$$

(6)

The voltage across the capacitor  $C_2$  is -

$$V_{C_2} = \frac{C_1 V}{C_1 + C_2}$$

Substituting 4  $\mu F$  for  $C_1$ , 2  $\mu F$  for  $C_2$   
and 300 V for  $V$ , we get -

$$V_{C_2} = \left( \frac{4 \mu F}{2 \mu F + 4 \mu F} \right) \times 300 V$$

$$= 200 V$$

Using Kirchhoff's loop rule to the  
closed circuit junctions  $B$  and  $D$  in the  
figure given in the question, we get -

$$-V_{C_1} - (V_E - V_D) + V_{C_2} = 0$$

$$V_E - V_D = V_{C_2} - V_{C_1}$$

Substituting 100 V for  $V_{C_1}$  and 200 V for  
 $V_{C_2}$  -

$$V_E - V_D = 200 V - 100 V$$

$$= 100 V$$

(7)

The potential difference between D & E is 100V

∴

- (d) The capacitor 4μF and 2μF are connected in parallel on both sides when the switch is closed.

$$C_{24} = 4\mu F + 2\mu F \\ = 6\mu F$$

The voltage across the point E is

$$V_E = \left( \frac{C_{24}}{C_{24} + C_{27}} \right) V$$


Substituting 6μF for  $C_{24}$  and 300V for V.

$$V_E = \left( \frac{6\mu F}{6\mu F + 6\mu F} \right) (300V)$$

$$= 150V$$

∴ The potential at point E after the switch is closed is 150V.

∴

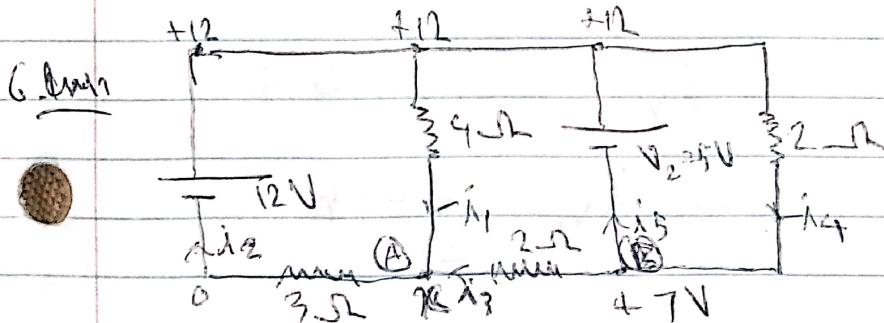

(8)

By nodal analysis, for calculating the potential 'x' at point 'A':

$$\frac{(12-7)}{2} + \frac{(x-12)}{4} + \frac{(x-0)}{3} = 0$$

$$\frac{6(x-7) + 3(x-12) + 4x}{12} = 0$$

$$6x - 42 + 3x - 36 + 4x = 0$$

$$13x = 78 \\ x = 6V$$

(a)  $i_2 = \frac{6-0}{3} = 2 \text{ amp}$

$$i_3 = \frac{12-6}{4} = \frac{3}{2} \text{ amp} = 1.5 \text{ amp.}$$

$$i_4 = \frac{i_2 - i_3}{2} = 0.5 \text{ amp.}$$

$$i_5 = i_2 + i_3 = 2.5 \text{ amp.}$$

At point 'B',  $i_4 = i_5 + i_3$

$$i_5 = 2.5 - 0.5$$

$$\therefore i_5 = 2 \text{ amp.}$$

(9)

(b) Power supplied by  $V_1$  :-

$$P_1 = 12 \times 2 = \underline{24} \text{ watt}$$

Power supplied by  $V_2$  :-

$$P_2 = 5 \times 2 = \underline{10} \text{ watt}$$